

Capacitors Circuits

James H Dann, Ph.D.

To access the online version of this FlexBook
click the link below:

https://www.ck12.org/c/physics/capacitor-circuits/lesson/Capacitors-Circuits-PPC/?referrer=concept_details

To access a customizable version of this book, as well as other interactive content, visit www.ck12.org

CK-12 Foundation is a non-profit organization with a mission to reduce the cost of textbook materials for the K-12 market both in the U.S. and worldwide. Using an open-source, collaborative, and web-based compilation model, CK-12 pioneers and promotes the creation and distribution of high-quality, adaptive online textbooks that can be mixed, modified and printed (i.e., the FlexBook® textbooks).

Copyright © 2024 CK-12 Foundation, www.ck12.org

The names “CK-12” and “CK12” and associated logos and the terms “FlexBook®” and “FlexBook Platform®” (collectively “CK-12 Marks”) are trademarks and service marks of CK-12 Foundation and are protected by federal, state, and international laws.

Any form of reproduction of this book in any format or medium, in whole or in sections, must be attributed according to our attribution guidelines.

<https://www.ck12info.org/about/attribution-guidelines>

Except as otherwise noted, all CK-12 Content (including CK-12 Curriculum Material) is made available to Users in accordance with the CK-12 Curriculum Materials License

<https://www.ck12info.org/curriculum-materials-license>



Complete terms for use for the CK-12 website can be found at:
<http://www.ck12info.org/terms-of-use/>

Printed: February 22, 2024 (PST)



CONTRIBUTORS

Chris Addiego
Antonio De Jesus
López

AUTHORS

James H Dann, Ph.D.



Capacitor Circuits

Circuits containing capacitors are easy to understand, take a closer look at them.

Capacitors Circuits

When a capacitor is placed in a circuit, current does not actually travel across it. Rather, equal and opposite charge begins to build up on opposite sides of the capacitor --- mimicking a current --- until the electric field in the capacitor creates a potential difference across it that balances the voltage drop across any parallel resistors or the voltage source itself (if there are no resistors in parallel with the capacitor). The ratio of charge on a capacitor to potential difference across it is called capacitance.

It is important to break down a complicated circuit into the equivalent capacitance using the rules for capacitors in series and capacitors in parallel. Also remember that capacitors in parallel have the same voltage while capacitors in series have the same charge.

Key Equations


$$C = \frac{Q}{V} \quad \text{Definition of Capacitance}$$

$$C_{\text{parallel}} = C_1 + C_2 + C_3 + \dots \quad \text{Capacitors in parallel add like resistors in series}$$

$$\frac{1}{C_{\text{series}}} = \frac{1}{C_1} + \frac{1}{C_2} + \frac{1}{C_3} + \dots \quad \text{Capacitors in series add like resistors in parallel}$$

Example

In the circuit shown below, determine (a) the total capacitance and (b) the total charge stored.

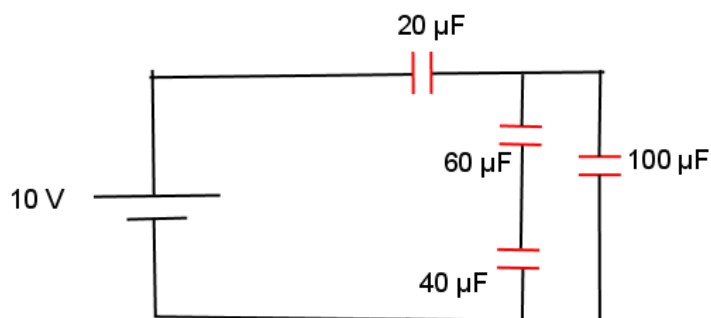

[Figure1]

(a): In solving this problem, we'll call the $20\ \mu\text{F}$ capacitor C_1 , the $60\ \mu\text{F}$ capacitor C_2 , the $40\ \mu\text{F}$ capacitor C_3 , and the $100\ \mu\text{F}$ capacitor C_4 .

Our first step will be to find the equivalent capacitance of C_2 and C_3 .

$$\begin{aligned}\frac{1}{C_{2,3}} &= \frac{1}{C_2} + \frac{1}{C_3} \\ \frac{1}{C_{2,3}} &= \frac{1}{60\ \mu\text{F}} + \frac{1}{40\ \mu\text{F}} \\ \frac{1}{C_{2,3}} &= \frac{5}{120\ \mu\text{F}} \\ C_{2,3} &= 24\ \mu\text{F}\end{aligned}$$

Next, we'll combine the capacitance of $C_{2,3}$ and C_4 .

$$\begin{aligned}C_{2,3,4} &= C_{2,3} + C_4 \\ C_{2,3,4} &= 24\ \mu\text{F} + 100\ \mu\text{F} \\ C_{2,3,4} &= 124\ \mu\text{F}\end{aligned}$$

Finally, we can combine $C_{2,3,4}$ with C_1 to find the total capacitance.

$$\frac{1}{C_{eq}} = \frac{1}{C_1} + \frac{1}{C_{2,3,4}}$$

$$\frac{1}{C_{eq}} = \frac{1}{20 \mu\text{F}} + \frac{1}{124 \mu\text{F}}$$

$$\frac{1}{C_{eq}} = .058 \mu\text{F}^{-1}$$

$$C_{eq} = 17.22 \mu\text{F}$$

(b): Now we can use this value to find the total charge stored on all the capacitors by also using the voltage provided on the diagram.

$$Q = CV$$

$$Q = 17.22 \mu\text{F} * 10 \text{ V}$$

$$Q = 172.2 \mu\text{C}$$

Capacitor Problem

For the diagram to the left, let $R=100 \text{ ohms}$, $C_1=6 \text{ micro Farads}$ and $C_2=24 \text{ micro Farads}$ and the Voltage is 30 V . Initially the capacitors are uncharged.


- a. What is the Voltage difference across C_1 0V
- b. Now, switch S_1 is closed. Determine the charge on C_1 when equilibrium is reached. 180 μC
- c. Next S_2 is opened and switch S_2 is closed. Determine the charge on C_2 when equilibrium is again reached.
- d. S_2 remains closed and now S_1 is also closed. How much additional charge flows from the battery?

ck-12

James Dann

<https://www.ck12.org/flx/render/embeddedobject/335>

Review

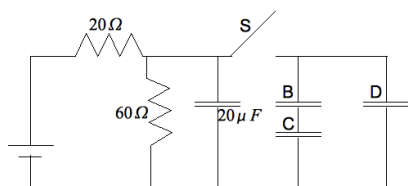

[Figure2]

1. Consider the figure above with switch, S , initially open and the power supply set to 24 V:
 - a. What is the voltage drop across the 20Ω resistor?
 - b. What current flows thru the 60Ω resistor?
 - c. What is the voltage drop across the 20 microfarad capacitor?
 - d. What is the charge on the capacitor?
 - e. How much energy is stored in that capacitor?
 - f. Find the capacitance of capacitors B , C , and D if compared to the $20\mu\text{F}$ capacitor where...
 - i. B has twice the plate area and half the plate separation
 - ii. C has twice the plate area and the same plate separation
 - iii. D has three times the plate area and half the plate separation
2. Now the switch in the previous problem is closed.
 - a. What is the total capacitance of branch with B and C?
 - b. What is the total capacitance of the circuit?
 - c. What is the voltage drop across capacitor B ?

Review (Answers)

1. a. 6V b. 0.3A c. 18V d. $3.6 \times 10^{-4}\text{C}$ e. $3.2 \times 10^{-3}\text{J}$ f. i) $80\mu\text{F}$ ii) $40\mu\text{F}$ iii) $120\mu\text{F}$
 2. a. $26.7\mu\text{F}$ b. $166.7\mu\text{F}$
-

1.0 REFERENCES

Image	Attributions
	License: CC BY-NC
	License: CC BY-NC